
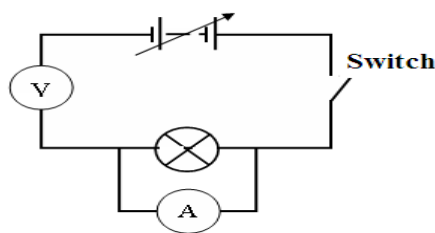


## Y11 PHYSICS WORKSHEET 7

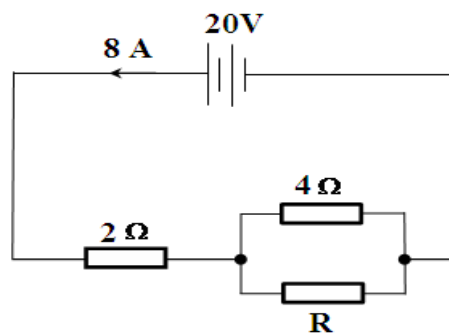7. (a) A charge of  $400\mu\text{C}$  passes a point in a conductor in 5 milliseconds.  
Find the current in the conductor.
- (b) State at least two units for electrical power.
- (c) A 20 W fluorescent desk lamp is being used for 5 hours each night for 10 weeks.
- (i) How much electrical energy (kWh) is used?
- (ii) Calculate the electrical bill for using the above at \$0.34 per kWh with 9% VAT?
- (d) To measure the resistance of a light bulb, a group of Physics students set up the circuit shown below.



- (i) Identify **one** error with the above set-up.
- (ii) After correcting their mistakes, the students switched on the circuit and obtained the following readings:  
Voltmeter reading = 0.3 V  
Ammeter reading = 0.2 A
- Find the resistance of the light bulb.
- (e) Use information given below in the circuit diagram to answer the questions.



Given that 8A current leaves the battery, find

- (i) the total resistance of the circuit.
- (ii) the potential difference across the  $2\Omega$  resistor.
- (iii) the potential difference across the  $4\Omega$  resistor.
- (iv) the current through the  $4\Omega$  resistor.
- (v) the current through the resistor R.
- (vi) the value of the resistor R.